



FACULTY OF ENGINEERING AND TECHNOLOGY
ELECTRICAL AND COMPUTER ENGINEERING DEPARTMENT
ADVANCED DIGITAL DESIGN ENCS3310

COURSE PROJECT

Prepared By : Zakiya AbuMurra

ID : 1191636

Instructor : D. Abdallatif Abuissa

Section : 1

BIRZEIT

June 12, 2022

Introduction

The aim of this project is to implement two digit BCD adder structural in two ways. One way is a ripple adder that a present stage wait carry out of previous stage, another one is a Carry look ahead that no dependently in carry out . Gradually , we built one bit full adder , four bit full adder , one digit BCD adder down to two digit BCD adder .

BCD adder is add two in input in binary number and check if the output greater than 9 or not to add 6 .In other word . to convert the result of operation to decimal that can people more familiar with the system ,

Then , the design put under the verification to confirm the results .

Contents

Introduction.....	2
1. Background.....	5
1.1 Binary Adder.....	5
1.1.1 Ripple Adder.....	5
1.1.2 Look Ahead Adder.....	6
1.2 BCD Adder	7
2 Design.....	8
2.1 Stage One using Ripple Adder.....	8
2.1.1 One bit Full adder	8
2.1.2 Four bit Ripple adder	8
2.1.3 1-Digit BCD adder using Ripple adder.....	9
2.1.4 2-Digit BCD adder using Ripple adder.....	9
2.2 Stage two using carry look a head	10
2.2.1 full adder for carry look ahead.....	10
2.2.2 4-bit Carry look ahead adder.....	11
2.3 Design Verification.....	12
3 Result	13
3.1 Stage One using Ripple adder.....	13
3.2 Stage two using Carry look a head adder.....	13
4 Conclusion and future Work.....	18
5 References.....	19
6 Appendix.....	20
6.1 One bit adder :.....	20
6.2 four 1-bit ripple adder :	20
6.3 1-digit BCD adder :.....	20
6.4 2-digit BCD adder using ripple adder :	21

Table of figures :

<u>Figure 1 : 4-bit Ripple adder</u>	5
<u>Figure 2 : 4-bit-Carry-Look-ahead-Adder-Logic-Diagram[3]</u>	6
<u>Figure 3: BCD summation</u>	7
<u>Figure 4 : One Bit Full adder design</u>	8
<u>Figure 5 : 4-bit Ripple Adder desgin</u>	9
<u>Figure 6 : 1-digit BCD using Ripple adder design</u>	9
<u>Figure 7 : 2-digit BCD using Ripple adder design</u>	10
<u>Figure 8 : full adder for carry look a head design</u>	10
<u>Figure 9 : 1-digit BCD using carry look ahead adder design</u>	11
<u>Figure 10: 2-digit BCD using carry look ahead adder design</u>	11

1. Background

1.1 Binary Adder

A binary adder is a digital circuit that performs the arithmetic addition of two binary values of arbitrary length.[1]

1.1.1 Ripple Adder

The ripple adder is a combinational circuit which add two n-bit binary number by using n-full adder block . this type is a parallel circuit because the adder block depend to the previous carry that cause a long propagation delay . This carry propagation causes a considerable time delay when n is large. [2]

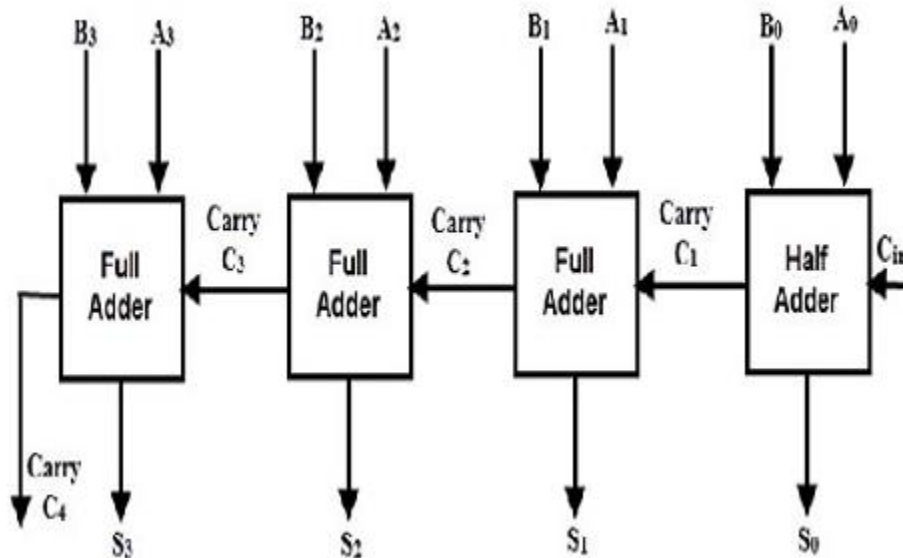


Figure 1 : 4-bit Ripple adder

1.1.2 Look Ahead Adder

we use this type of adder to reduce the propagation delay that occur during the addition operation by use the complex hardware circuitry .The carry output at any stage is dependent only on the initial carry bit of the beginning stage

From the truth table of the look-ahead adder , the Boolean expressions are :

Using the G_i and P_i terms the Sum S_i and Carry C_{i+1} are given as below where $G_i (A_i \oplus B)$ is a Carry generate and $P_i (A_i . B)$ is a carry propagate .

$$S_i = P_i \oplus G_i.$$

$$C_{i+1} = C_i.P_i + G_i.$$

Then ,the Carry Out for each full adder block is calculated as :

- $C_1 = C_0.P_0 + G_0.$
- $C_2 = C_1.P_1 + G_1 = (C_0.P_0 + G_0).P_1 + G_1.$
- $C_3 = C_2.P_2 + G_2 = (C_1.P_1 + G_1).P_2 + G_2.$
- $C_4 = C_3.P_3 + G_3 = C_0.P_0.P_1.P_2.P_3 + P_3.P_2.P_1.G_0 + P_3.P_2.G_1 + G_2.P_3 + G_3.[3]$

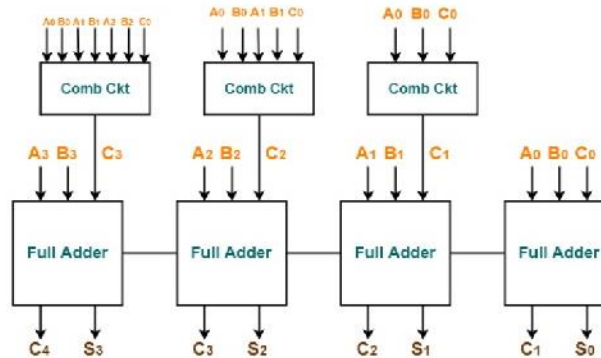


Figure 2 : 4-bit-Carry-Look-ahead-Adder-Logic-Diagram

1.2 BCD Adder

Although the binary number system is the most natural for a computer since it is easily represented in today's electronic technology, the decimal system is more familiar to most people. Converting decimal numbers to binary, performing all arithmetic calculations in binary, and then converting the binary outputs back to decimal is one technique to address this difference. This method demands the storage of decimal numbers in the computer in order to convert them to binary. Because the computer can only handle binary numbers, we must represent decimal digits using a code consisting of 1s and 0s. When decimal numbers are stored in a computer in coded form, it is also possible to perform arithmetic operations directly on them. [4]

the addition of two decimal digits in BCD, as well as the possibility of a carry from a prior pair of digits that were less significant. Because each digit cannot exceed 9, the total cannot exceed $9 + 9 + 1 = 19$, with the 1 representing a previous carry

For example , if we want add $(184 + 576)$ the result equal to 760 , we can do it in BCD adder as bellow :

1	1		
0001	1000	0100	
			+
0101	0111	0110	
<hr/>			
0111	10000	1010	Binary Sum
			+6
	0110	0110	
<hr/>			
0111	0110	0000	BCD sum
7	6	0	

Figure 3: BCD summation

Note that if the result of Binary summation greater than 9 , then add $(0110)_2$ to get in BCD sum .

2 Design

2.1 Stage One using Ripple Adder

2.1.1 One bit Full adder

In this part , we built the one bit full adder from AND , XOR and OR gates as shown in figure () There is three inputs (X , Y and Cin) and two output (s , Cout) where s is a summation result and Cout the Carry out from operation . We connect the gates together using wire that it wired output of gate to input of another gate. Each gate has a delay time, for two AND gates and one OR gate need respectively 8ns, 8ns, 8ns to get the carry out (Cout) result. Also, two OR gates need 24ns where each OR gate has a 12 ns time delay. Hence, all time delay for one bit full adder is 24ns. Where this value use later in Four bit Ripple adder .

Go to appendix No (1) to see code.

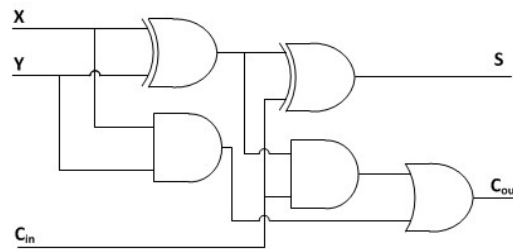


Figure 4 : One Bit Full adder design

2.1.2 Four bit Ripple adder

In this part , we have 4 one-bit full adder blocks. Each blocks has 3-bit Xi , Yi , Ci inputs and 2-bit Si , Coi output , then Call the module One bit full adder four times and connected together by wires . As we mentioned below , one block has 24ns time delay to get the correct answer so we add this value when call the blocks in code

You can see code in appendix No(2)

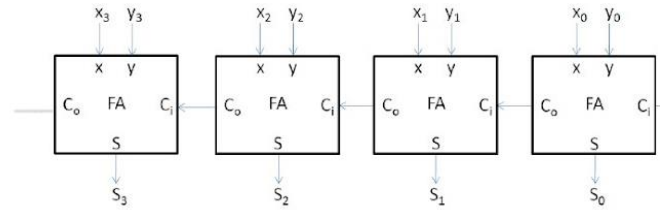


Figure 5 : 4-bit Ripple Adder desgin

2.1.3 1-Digit BCD adder using Ripple adder

In this part , we have a two input , each of them has a four bit , then these inputs enter 4-bit Ripple adder block, the output of this block enter as a input of anther 4-bit ripple adder block to convert the result form binary sum to BCD sum . Also, we can note the Combinational circuit content the two AND gates and OR gate which check if the binary sum in BCD sum form or not by add a (0, twice of carry out form combinational circuit) . In case the check is not the circuit will add (0110) to the binary sum.

You can see the code in appendix No (3).

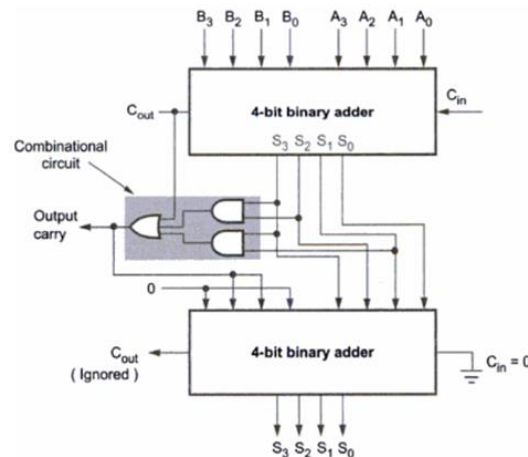


Figure 6 : 1-digit BCD using Ripple adder design

2.1.4 2-Digit BCD adder using Ripple adder

In this part, we built the two digit BCD adder using Ripple adder. Where have two inputs each of them has 8-bit. However, the input concatenate to be one input then enters to the register that implemented as a D-flip flop. As we know, the register has one input, clock and reset and output which aim of register is store the data.

In the code we implement one module for registers and we use the parameter to allow use it more than one in different number of bits.

You can see the code in appendix No (4).

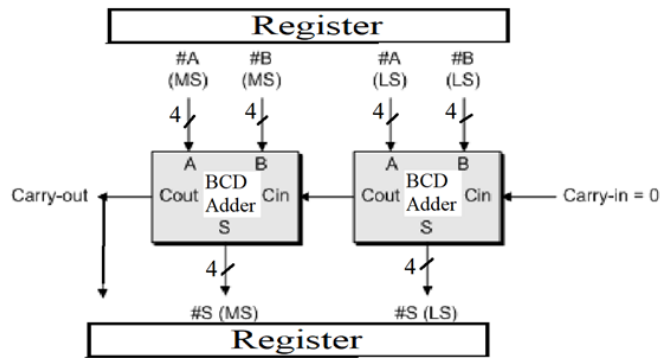


Figure 7 : 2-digit BCD using Ripple adder design

2.2 Stage two using carry look a head

2.2.1 full adder for carry look ahead

The carry look ahead adder was built using modified the full-adder. They both provide the same inputs . The Cout output in full adder has been replaced with carry propagate and generate in carry look ahead since the carry-out output isn't necessary, but the carry propagate and generate outputs are

The carry-in determines overall production, although P and G are created separately. . So , the propagation delay was reduced .

You can see the code in appendix No(7).

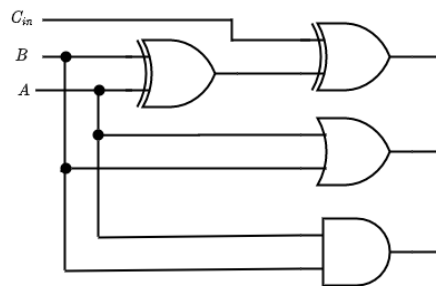


Figure 8 : full adder for carry look a head design

2.2.2 4-bit Carry look ahead adder

In this part , because of complexity for the circuit gate level , we implemented the summation , carry out , carry generate and carry propagate using gates based on the Boolean expressions that derived from truth table that mentioned in 1.1.2 . In addition . the total delay for all system using carry look ahead adder is 128ns , that reduce the propagation delay when use ripple adder .

You can see the code in appendix no(8).

2.2.3 1-digit BCD using carry look ahead :

This part explain same as 2.1.4 , but the different in implementation use a carry look ahead adder in binary adder .

You can see the code in appendix no (9)

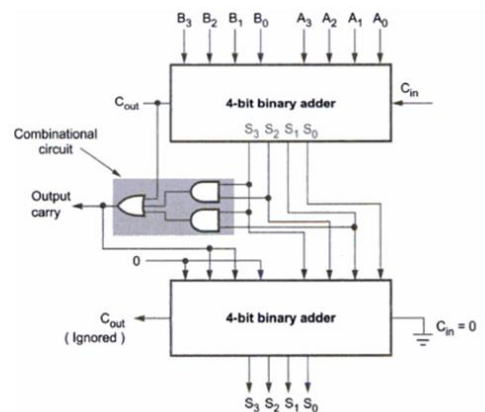


Figure 9 : 1-digit BCD using carry look ahead adder design

2.2.4 2-digit BCD using carry look ahead adder

All performance for the system will improved because the carry look ahead adder reduce the propagation delay to 128ns .

You can see the code in appendix no(10)

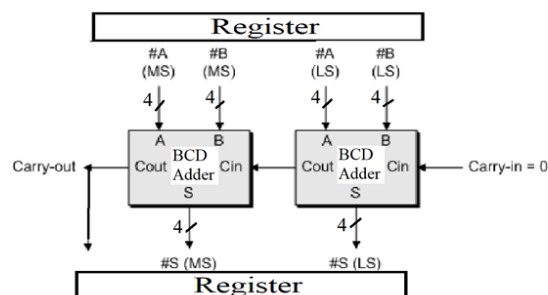


Figure 10: 2-digit BCD using carry look ahead adder design

2.3 Design Verification

In Design Verification , test inputs were generated on rising edges, and the predicted outputs were built behaviorally in the test generator to verify the design. On every clock cycle, the circuit outputs are compared to the predicted ones for a result analyzer, and if there is a mismatch, a warning message is presented. A test bench is used to give a clock the appropriate delay for system latency, as well as inputs generated, which are then passed to the circuit, and outputs are then passed to the result analyzer, from which both behavior and structure are derived.

2.3.1 Test generator

In this part , the code built behavior that has inputs and outputs . we add 6 if the result from or and AND operation equals to 1 . you can see all detail in appendix no (11)

2.3.2 Analyzer

In this part, correct values are compared with output values, if they are not equal then an error is asserted, and an error message is printed.

You can see code in appendix no(12).

2.3.3 Test bench

All of the components are connected here by creating test inputs, passing them to the comparator circuit, and comparing the results to the expected ones to determine whether there is an error.

You can see test bench for stage one using the ripple adder in appendix no(13).


And for stage two using the look ahead carry in appendix no(14).

3 Result

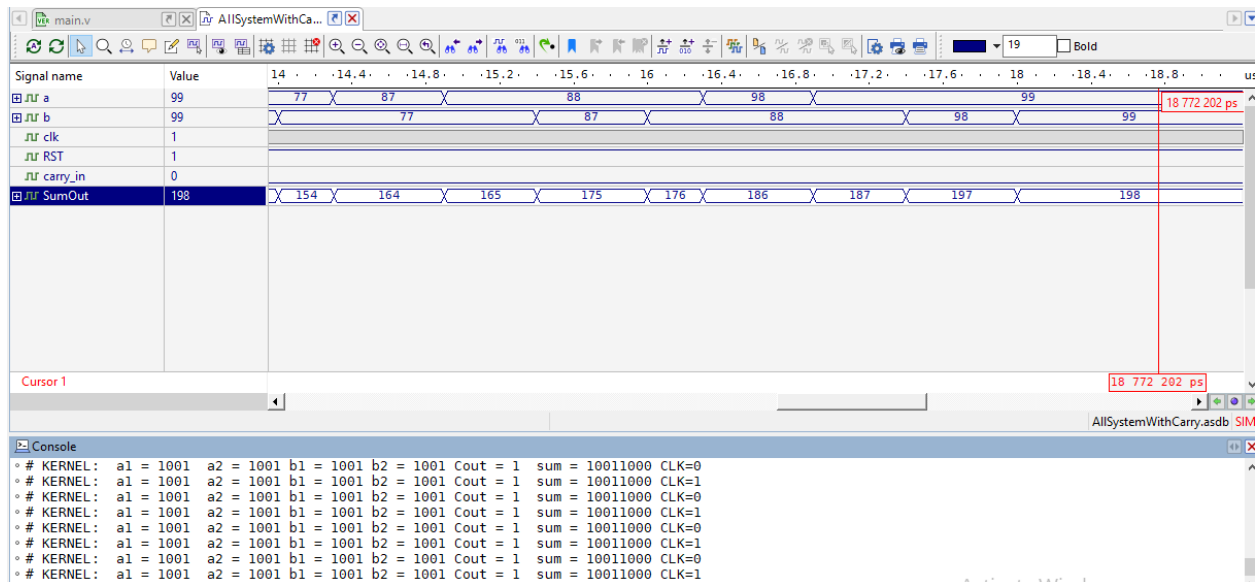3.1 Stage One using Ripple adder

Using test bench code then simulate the module . taking the example , if $a(\text{input}) = 99$ in decimal that equal $(1001\ 1001)$ in binary and $b(\text{input}) = 99$ in decimal that equal $(1001\ 1001)$ in binary . the output equal to 198 in decimal that represent $(0001\ 1001\ 1000)_2$ where the carry out from the addition is (0001) . the results confirm what we explain in part 1.2 .


You can see the test bench code in appendix No(6) .



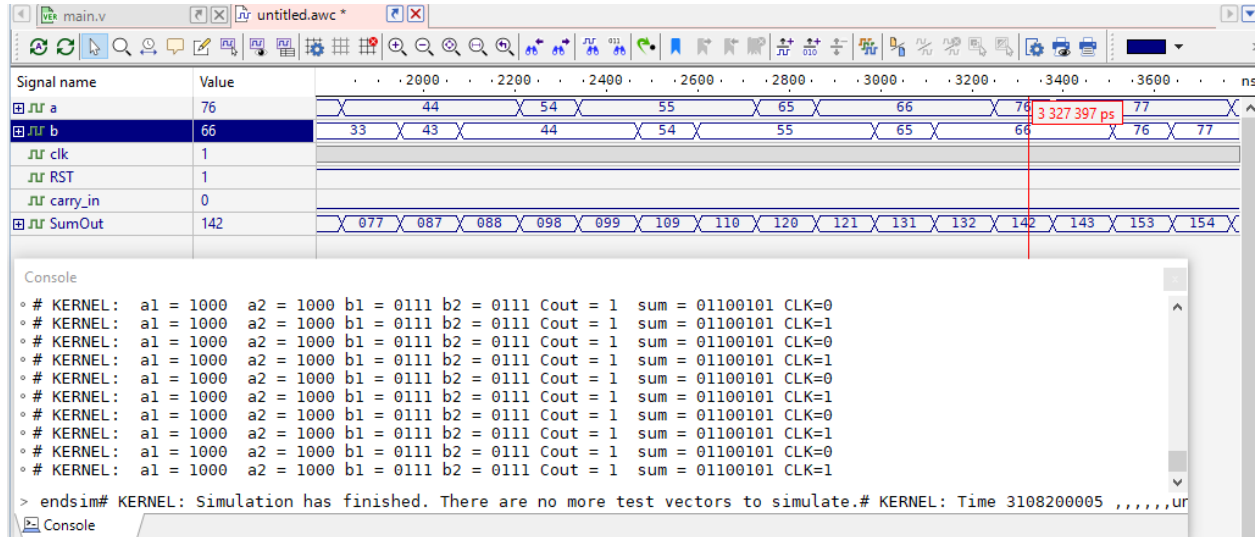3.2 Stage two using Carry look a head adder

Using test bench code then simulate the module . taking the example , if $a(\text{input}) = 76$ in decimal that equal $(0111\ 0110)$ in binary and $b(\text{input}) = 66$ in decimal that equal $(0110\ 0110)$ in binary . the output equal to 142 in decimal that represent $(0001\ 0100\ 0010)_2$ where the carry out from the addition is (0001) . the results confirm what we explain in part 1.2 .


You can see the test bench code in appendix no(15) :



3.2 Verification testing

3.2.1 Testing without error for stage one :

We note all is correct .

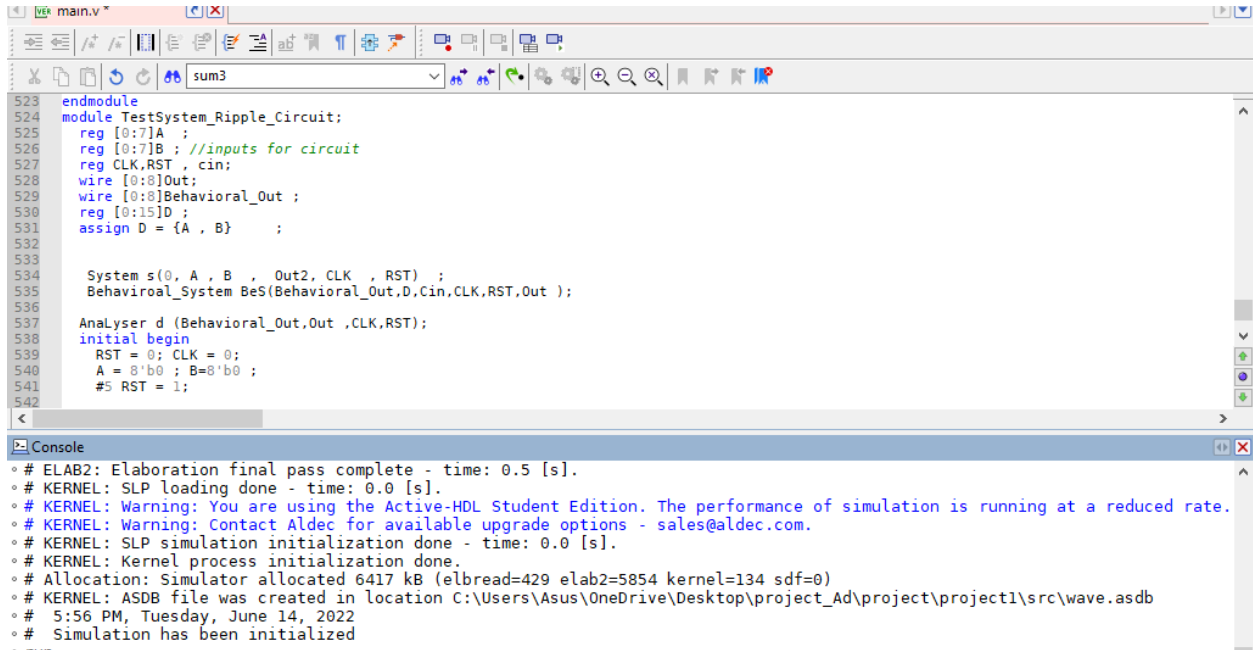

```
523 endmodule
524 module TestSystem_Ripple_Circuit;
525     reg [0:7]A ;
526     reg [0:7]B ; //inputs for circuit
527     reg CLK,RST , cin;
528     wire [0:8]Out;
529     wire [0:8]Behavioral_Out ;
530     reg [0:15]D ;
531     assign D = {A , B} ;
532
533
534     System s(0, A , B , Out2, CLK , RST) ;
535     Behavioraol_System BeS(Behavioral_Out,D,Cin,CLK,RST,Out );
536
537     Analyser d (Behavioral_Out,Out ,CLK,RST);
538     initial begin
539         RST = 0; CLK = 0;
540         A = 8'b0 ; B=8'b0 ;
541         #5 RST = 1;
542
543
544
999
```

```
Console
*# ELAB2: Elaboration final pass complete - time: 0.5 [s].
*# KERNEL: SLP loading done - time: 0.0 [s].
*# KERNEL: Warning: You are using the Active-HDL Student Edition. The performance of simulation is running at a reduced rate.
*# KERNEL: Warning: Contact Aldec for available upgrade options - sales@aldec.com.
*# KERNEL: SLP simulation initialization done - time: 0.0 [s].
*# KERNEL: Kernel process initialization done.
*# Allocation: Simulator allocated 6417 kB (elbread=429 elab2=5854 kernel=134 sdf=0)
*# KERNEL: ASDB file was created in location C:\Users\Asus\OneDrive\Desktop\project_Ad\project\project1\src\wave.asdb
*# 5:56 PM, Tuesday, June 14, 2022
*# Simulation has been initialized
```

Figure 11 : design verification for ripple BCD adder without error

3.2.2 Testing with error for stage one :

If we change any gates from code that caused the result is error . the analyzer will be print error as shown in figure (12).

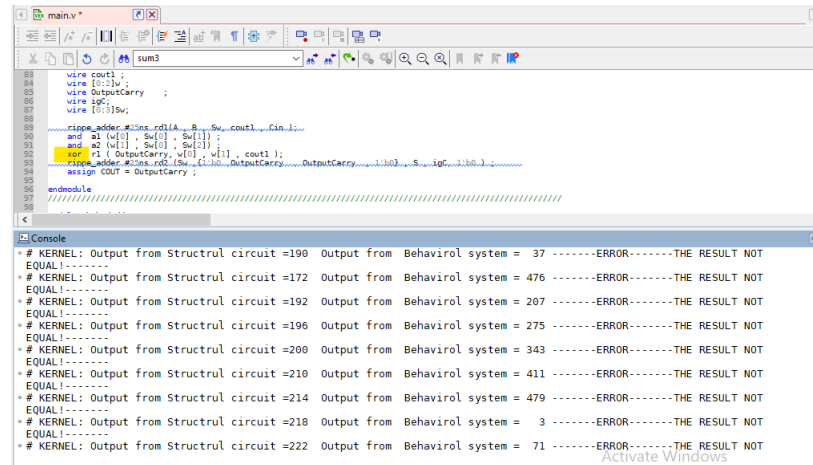


Figure 12: design verification for ripple BCD adder with error

3.2.3 Testing without error for stage two :

No messages error as shown below in figure 13.


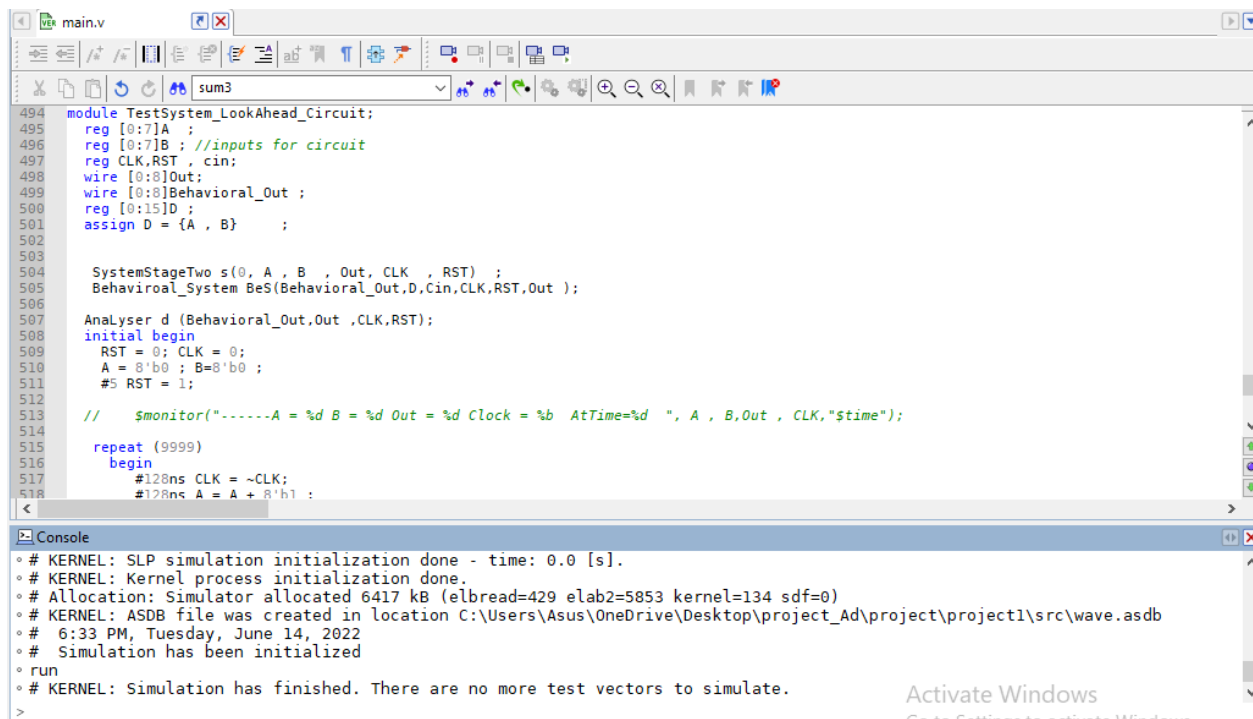


Figure 13 : design verification for Carry look ahead BCD adder without error

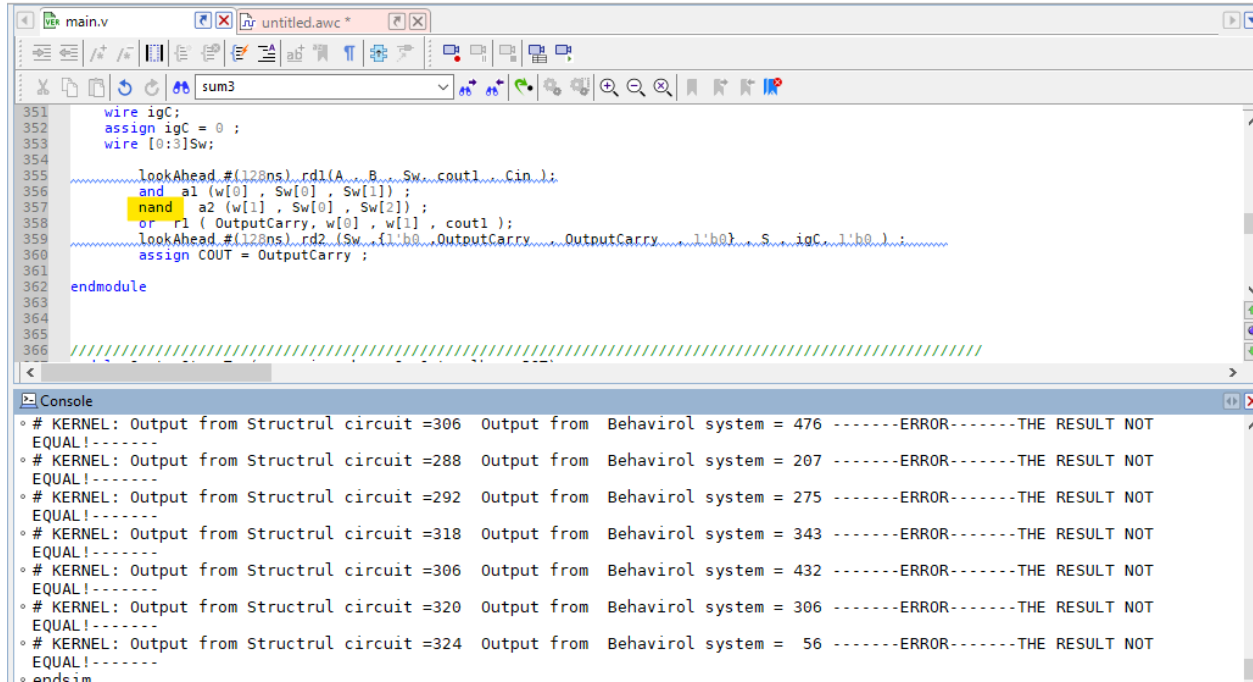3.2.4 Testing with error

If we change any gates from code that caused the result is error . the analyzer will be print error as shown in figure (14).



The screenshot shows a Verilog code editor with a file named 'main.v' and a circuit named 'sum3'. The code defines a BCD adder with two 4-bit inputs 'a' and 'b', and a carry-in 'cin'. It uses a 4-bit output 'cout' and a 4-bit output 'sum'. The code is as follows:

```
351 wire igC;  
352 assign igC = 0 ;  
353 wire [0:3]Sw;  
354  
355 lookAhead #(128ns) rd1(A , B , Sw , cout1 , Cin );  
356 and a1 (w[0] , Sw[0] , Sw[1]);  
357 nand a2 (w[1] , Sw[0] , Sw[2]);  
358 or r1 ( OutputCarry , w[0] , w[1] , cout1 );  
359 lookAhead #(128ns) rd2 (Sw , f1'b0 , OutputCarry , OutputCarry , 1'b0 , S , igC , 1'b0 );  
360 assign COUT = OutputCarry ;  
361  
362 endmodule  
363  
364  
365  
366
```

The console window shows the following output:

```
Console  
# KERNEL: Output from Structrul circuit =306 Output from Behavirol system = 476 -----ERROR-----THE RESULT NOT  
EQUAL!-----  
# KERNEL: Output from Structrul circuit =288 Output from Behavirol system = 207 -----ERROR-----THE RESULT NOT  
EQUAL!-----  
# KERNEL: Output from Structrul circuit =292 Output from Behavirol system = 275 -----ERROR-----THE RESULT NOT  
EQUAL!-----  
# KERNEL: Output from Structrul circuit =318 Output from Behavirol system = 343 -----ERROR-----THE RESULT NOT  
EQUAL!-----  
# KERNEL: Output from Structrul circuit =306 Output from Behavirol system = 432 -----ERROR-----THE RESULT NOT  
EQUAL!-----  
# KERNEL: Output from Structrul circuit =320 Output from Behavirol system = 306 -----ERROR-----THE RESULT NOT  
EQUAL!-----  
# KERNEL: Output from Structrul circuit =324 Output from Behavirol system = 56 -----ERROR-----THE RESULT NOT  
EQUAL!-----  
endcsm
```

Figure 14 : design verification for Carry look ahead BCD adder with error

3 Conclusion and future Work

In Our project , the Two digit BCD adder was built in two ways . Using ripple adder and carry ahead adder . In each way we implement the design structural using gate level .Which takes me to be able handle the correct delay time for each circuit. In addition , if I had to choose only one approach for constructing the BCD ADDER circuit, I would choose the carry look ahead adder because it gives the results quickly .

The future work can be resolve several problem as redundant the code . for example , the full adder can using in ripple and carry ahead if the architecture for it have the mux to choose the specific gates .

This project served as a springboard for us to enter the domains of hardware design and verification. I had a great time working on it, and I'd like to do more research and stay up with new developments. Because I believe that 'improvements, not excuses,' is the key.

4 **References**

1. <https://www.tutorialspoint.com/what-is-binary-adder> [accessed 13 June 2022 at 6:00pm]
2. <https://www.gatevidyalay.com/ripple-carry-adder/> [accessed June 13, 2022 at 6:15pm]
3. <https://www.elprocus.com/carry-look-ahead-adder/> [accessed June 13, 2022 at 5:00pm]
4. https://drive.google.com/file/d/115Otrw7LO2JhUWrH4GYEqvk_MBqQTYb_/view[accessed June 13, 2022 at 10:00pm]

5 Appendix

5.2 One bit adder :

```
////////////////////////////////////
module fulladder_oneBit(X, Y, Ci, SUM, COUT);

    input X, Y, Ci;
    output SUM, COUT;
    wire w1,w2,w3;

    xor (w1, X, Y);
    xor (SUM, w1, Ci);
    and (w2, w1, Ci);
    and (w3, X, Y);
    or  (COUT, w2, w3);

endmodule
////////////////////////////////////
```

5.3 four 1-bit ripple adder :

```
////////////////////////////////////
module rippe_adder(X, Y, S, Co , Cin);
    input [0:3] X;
    input [0:3]Y;// Two 4-bit inputs
    input Cin ;
    output [0:3] S; //sum
    output Co; // carry out
    wire w1, w2, w3;
    //calling 4 1-bit full adders to design 4-bit ripple adder
    fulladder_oneBit #25ns u1(X[3], Y[3], Cin, S[3], w1);
    fulladder_oneBit #25ns u2(X[2], Y[2], w1, S[2], w2);
    fulladder_oneBit #25ns u3(X[1], Y[1], w2, S[1], w3);
    fulladder_oneBit #25ns u4(X[0], Y[0], w3, S[0], Co);
endmodule
```

5.4 1-digit BCD adder :

```
////////////////////////////////////
module BCD (A , B ,Cin , COUT , S ) ;
    input [0:3]A ;
    input [0:3]B ;
    input Cin ;
    output COUT ;
    output [0:3]S ;
    wire cout1 ;
    wire [0:2]w ;
    wire OutputCarry ;
    wire igC;
    wire [0:3]Sw;

    rippe_adder #25ns rd1(A , B , Sw, cout1 , Cin );
    and a1 (w[0] , Sw[0] , Sw[1]);
    and a2 (w[1] , Sw[0] , Sw[2]);
    or r1 ( OutputCarry, w[0] , w[1] , cout1 );
    rippe_adder #25ns rd2 (Sw ,{1'b0 ,OutputCarry , OutputCarry , 1'b0} , S , igC, 1'b0 );
    assign COUT = OutputCarry ;

endmodule
////////////////////////////////////
```

5.5 2-digit BCD adder using ripple adder :

```
module Reg2(D,clk,rest , Out2);
parameter n = 1;

input [n-1:0]D;
input clk , rest ;
output reg [n-1:0] Out2;

always @ (posedge clk or negedge rest)
if (!rest)
    Out2 <= 0;
else
    Out2 <= D;

endmodule

////////////////////////////////////
module System(carry_in,a,b , SumOut, clk , RST);
input carry_in;
input [0:7] a;
input [0:7] b;
input clk , RST ;
output [0:8]SumOut ;
wire Carry_out;
wire [0:15]q, R ;
wire [0:7]out;
wire cout;
wire [0:8]CarryWithout ;

assign q ={a,b};

Reg2 reg1(q,clk, RST,R);
defparam reg1.n = 16;

BCD b1(R[4:7], R[12:15] , 1'b0 , cout , out[4:7] );
BCD b2(R[0:3], R[8:11] ,cout , Carry_out , out[0:3] );
assign CarryWithout = { Carry_out , out };
Reg2 #180ns reg2 ( CarryWithout , clk , RST, SumOut ) ;
defparam reg2.n = 9;

endmodule
```

5.6 Test Bench for Stage One :

```
77 endmodule
78
79 module tb_system ;
80
81     reg [0:7]a ;
82     reg [0:7]b;
83     reg clk ;
84     reg RST ;
85     reg carry_in ;
86
87     wire [0:8]SumOut;
88
89     System s (carry_in,a,b , SumOut, clk , RST);
90
91     always #600 clk = ~ clk ;
92
93     initial
94     begin
95         clk =0 ;   RST =1 ; a =0 ; b =0 ;   carry_in=0 ;
96
97
98         $monitor (" a1 = %b  a2 = %b b1 = %b b2 = %b Cout = %b  sum = %b CLK=%b" , a[0:3], a[4:7] , b[0:3] , b[4:7], SumOut[0],SumOut[1:8] , clk );
99     repeat(9)
100     begin
101         #300ns a[0:3] = a[0:3] + 1 ;
102         #600ns a[4:7] = a[4:7] + 1 ;
103         #500ns b[0:3] = b[0:3] + 1;
104         #600ns b[4:7] = b[4:7] + 1;
105     end
106 end
107
108
```

Activate Windows

5.7 full adder for carry look ahead

```
273
274 module FaLook(a,b,cin,s,p,g);
275     input a,b,cin;
276     output s,p,g;
277     wire wxor;
278     xor(wxor,a,b);
279     or (p,a,b);
280     and (g,a,b);
281     xor(s,wxor,cin);
282 endmodule
```

5.8 4-bit Carry look ahead adder

```
////////////////////////
module lookAhead(a,b,sum , cout , cin);
    input [0:3]a;
    input [0:3]b;
    input cin;
    output cout;
    output [0:3]sum;
    wire[0:21] wires;

    FaLook FA0 (a[3],b[3],cin,sum[3],wires[21],wires[20]);
    and(wires[19],cin,wires[21]);
    or(wires[18],wires[19],wires[20]);
    FaLook FA1(a[2],b[2],wires[18],sum[2],wires[17],wires[16]);
    and(wires[15],cin,wires[21],wires[17]);
    and(wires[14],wires[20],wires[17]);
    or(wires[13],wires[16],wires[14],wires[15]);
    FaLook FA2(a[1],b[1],wires[13],sum[1],wires[12],wires[11]);
    and(wires[10],cin,wires[21],wires[17],wires[12]);
    and(wires[9],wires[20],wires[17],wires[12]);
    and(wires[8], wires[16],wires[12]);
    or(wires[7],wires[11],wires[10],wires[9],wires[8]);
    FaLook FA3(a[0],b[0],wires[7],sum[0],wires[6],wires[5]);
    and (wires[4],cin,wires[21],wires[17],wires[12],wires[6]);
    and(wires[3],wires[20],wires[17],wires[12],wires[6]);
    and(wires[2],wires[16],wires[12],wires[6]);
    and(wires[1],wires[11],wires[6]);
    or(wires[0],wires[1],wires[2],wires[3],wires[4]);
    assign cout = wires[0];
endmodule
```

5.9 1-digit BCD using carry look ahead

```
///LOOK AHEAD BCD ADDER FOR STAGE TWO
module BCDStageTwo (A , B ,Cin , COUT , S ) ;
    input [0:3]A ;
    input [0:3]B ;
    input Cin ;
    output COUT ;
    output [0:3]S ;
    wire cout1 ;
    wire [0:2]w ;
    wire OutputCarry ;

    wire igC;
    assign igC = 0 ;
    wire [0:3]Sw;

    lookAhead #(128ns) rd1(A , B , Sw, cout1 , Cin );
    and a1 (w[0] , Sw[0] , Sw[1]) ;
    and a2 (w[1] , Sw[0] , Sw[2]) ;
    or r1 ( OutputCarry, w[0] , w[1] , cout1 );
    lookAhead #(128ns) rd2 (Sw ,{1'b0 ,OutputCarry , OutputCarry , 1'b0} , S , igC, 1'b0 ) ;
    assign COUT = OutputCarry ;

endmodule
```

5.10 2-digit BCD using carry look ahead adder

```

module SystemStageTwo(carry_in,a,b , SumOut, clk , RST);
input carry_in;
input [0:7] a;
input [0:7] b;
input clk ,RST ;
output [0:8]SumOut ;
wire Carry_out;
wire [0:15]q ;
wire [0:15]R ;
wire [0:7]out;
wire cout;
wire [0:8]CarryWithout ;

assign q ={a,b};

Reg2 reg1(q,clk, RST,R);
defparam reg1.n = 16;

BCDStageTwo b1(R[4:7], R[12:15] , 1'b0 , cout , out[4:7] ) ;
BCDStageTwo b2(R[0:3], R[8:11] ,cout , Carry_out , out[0:3] ) ;
assign CarryWithout = { Carry_out , out } ;

Reg2 #128ns reg21 ( CarryWithout , clk , RST, SumOut ) ;
defparam reg1.n = 8 ;

endmodule

```

5.11 Test Generator

```

Behaviroal_System(Out1,X,Cin,CLK,RST,Out2);

tput reg [0:8]Out1 ;
tput Out2 ;
put [0:15] X ;
put Cin,CLK,RST ;
g [0:3]SumOut1,SumOut2,SumOut3,SumOut4;
g carryOut1,carryOut2,carryOut3,carryOut4,carryOut5;

ways @(posedge CLK or negedge RST)
begin
{carryOut1,SumOut1} = X[0:3]+X[4:7];
carryOut2= (SumOut1[3] & SumOut1[2]) | (SumOut1[3] & SumOut1[1]) | carryOut1 ;
if(carryOut2)
begin

SumOut2 = SumOut1+4'b0110 ;
Out1[0:3] = SumOut2;

end
else
Out1[0:3] = SumOut1;

{carryOut3,SumOut3} = X[8:11]+X[12:15]+carryOut2;
carryOut4 = (SumOut3[3] & SumOut3[2]) | (SumOut3[3] & SumOut3[1]) | carryOut3 ;
if(carryOut4)
begin

SumOut4= SumOut3+4'b0110 ;
Out1[4:7] = SumOut4;

end
else
Out1[4:7] = SumOut3;
Out1[8] = carryOut4;

end
end

```


5.12 Analyzer

```
module AnaLyser(Behavioral_Out,Structural_Out,CLK,RST);
  input[0:8]Behavioral_Out,Structural_Out;
  input CLK,RST ;
  always @(posedge CLK or negedge RST)
  begin:beginAlways
    if(Behavioral_Out != Structural_Out)
    begin
      $display("Output from Structrul circuit =%d  Output from  Behavirol system = %d " , Structural_Out,Behavioral_Out);
    end
  end
endmodule
```

5.13 Test Bench for ripple system in Design verification

```
////////////////////////////////////
endmodule
module TestSystem_Ripple_Circuit;
  reg [0:7]A ;
  reg [0:7]B ; //inputs for circuit
  reg CLK,RST , cin;
  wire [0:8]Out;
  wire [0:8]Behavioral_Out ;
  reg [0:15]D ;
  assign D = {A , B} ;

  System s(0, A , B , Out2, CLK , RST) ;
  Behaviroal_System BeS(Behavioral_Out,D,Cin,CLK,RST,Out );

  AnaLyser d (Behavioral_Out,Out ,CLK,RST);
  initial begin
    RST = 0; CLK = 0;
    A = 8'b0 ; B=8'b0 ;
    #5 RST = 1;

    $monitor("A = %d B = %d Out = %d Clock = %b  AtTime ", A , B,Out , CLK,$time);

    repeat (9999)
    begin
      #128ns CLK = ~CLK;
      #128ns A = A + 8'b1 ;
      #128ns B = B + 8'b1 ;
    end
  end
endmodule
```

5.14 Test Bench for look ahead carry system in Design verification

```
module TestSystem_LookAhead_Circuit;
  reg [0:7]A ;
  reg [0:7]B ; //inputs for circuit
  reg CLK,RST , cin;
  wire [0:8]Out;
  wire [0:8]Behavioral_Out ;
  reg [0:15]D ;
  assign D = {A , B} ;

  SystemStageTwo s(0, A , B , Out, CLK , RST) ;
  Behaviroal_System BeS(Behavioral_Out,D,Cin,CLK,RST,Out );

  AnaLyser d (Behavioral_Out,Out ,CLK,RST);
  initial begin
    RST = 0; CLK = 0;
    A = 8'b0 ; B=8'b0 ;
    #5 RST = 1;

    $monitor("-----A = %d B = %d Out = %d Clock = %b  AtTime=%d -----ERROR-----THE RESULT NOT EQUAL!----- " , A , B,Out , CLK,$time");

    repeat (9999)
    begin
      #128ns CLK = ~CLK;
      #128ns A = A + 8'b1 ;
      #128ns B = B + 8'b1 ;
    end
  end
  //////////////////////////////////////
```

5.15 Test bench for Stage Two :

```
module tb_systemStageTwo ;
    reg [0:7]a ;
    reg [0:7]b;
    reg clk ;
    reg RST ;
    reg carry_in ;

    wire [0:8]SumOut;

    SystemStage s (carry_in,a,b , SumOut, clk , RST);
    always #128 clk = ~ clk ;

    initial
        begin
            clk =0 ;   RST =1 ; a =0 ; b =0 ;
            carry_in=0 ;

            $monitor (" a1 = %b , a2 = %b b1 = %b b2 = %b Cout = %b sum = %b CLK=%b" , a[0:3] , a[4:7] , b[0:3] , b[4:7] , SumOut[0],SumOut[1:8] , clk );
            //always #600 clk = ~ clk ;
            repeat(9) begin
                #128ns a[0:3] = a[0:3] + 1 ;
                #128ns a[4:7] = a[4:7] + 1 ;
                #240ns b[0:3] = b[0:3] + 1;
                #240ns b[4:7] = b[4:7] + 1;
            end
        end
endmodule
```

Activate Windows